



American Power Design, Inc.

"The best high voltage design solution"

SERIES OPERATION

Series Operation - Multiple Units

Using multiple units in series can be accomplished by placing a shunt diode on each unit, as seen in the circuit below. It is not recommended to go above the isolation voltage of any unit in the circuit.

